

DIY circuit

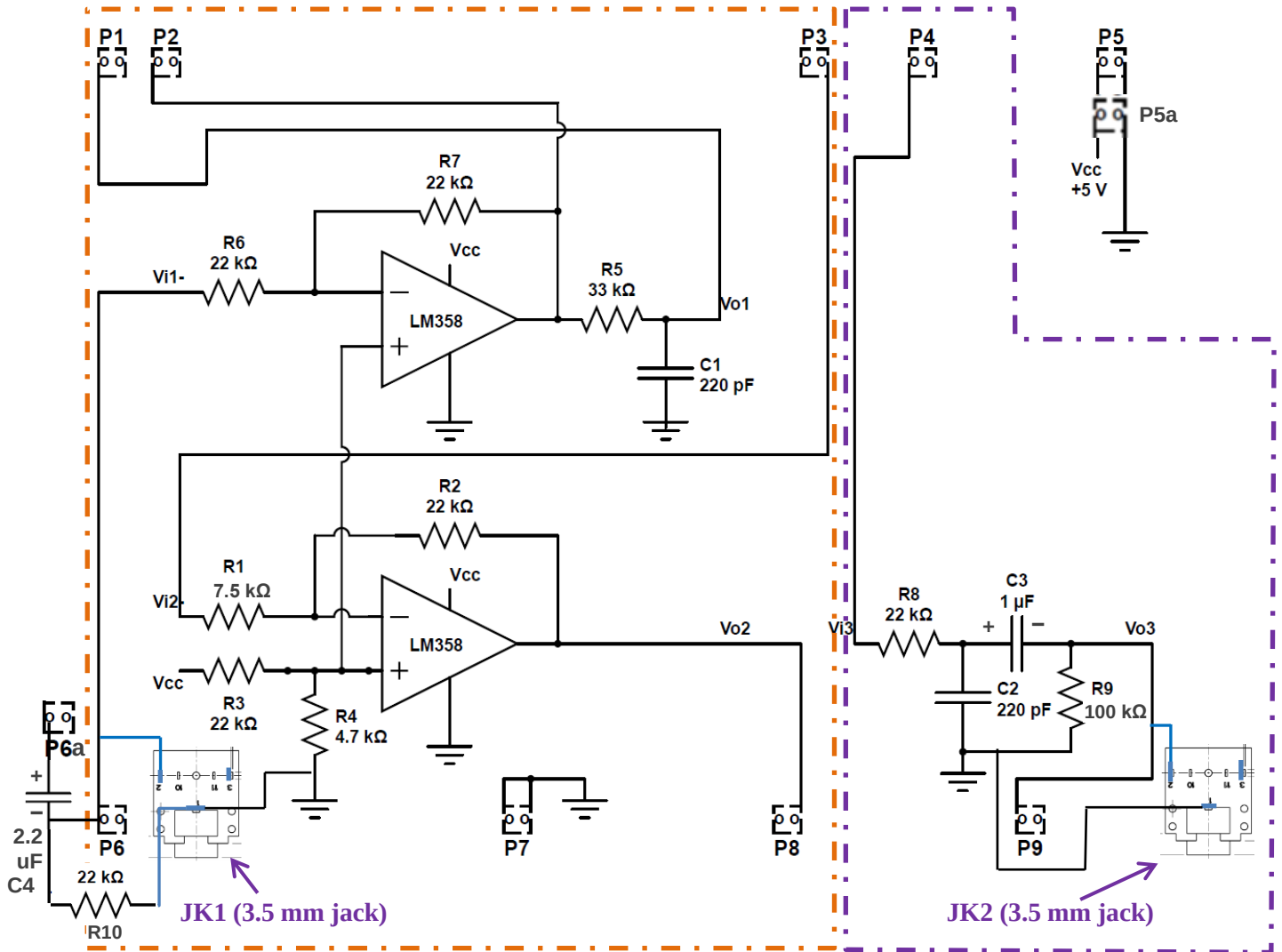


Fig. 1. The diagram of the DIY circuit.

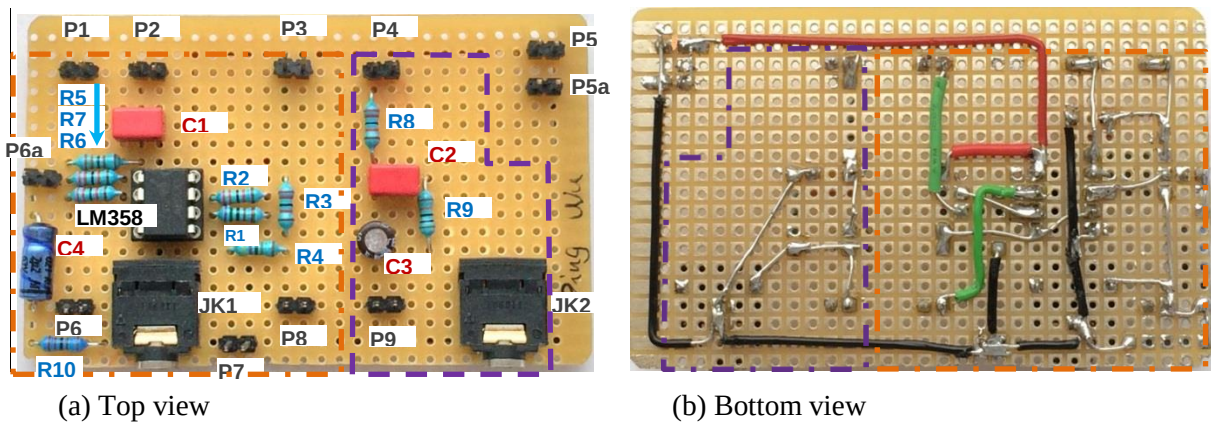


Fig. 2. The layout of the DIY circuit for the UC3-A3 evaluation kit. The black wires connect to the

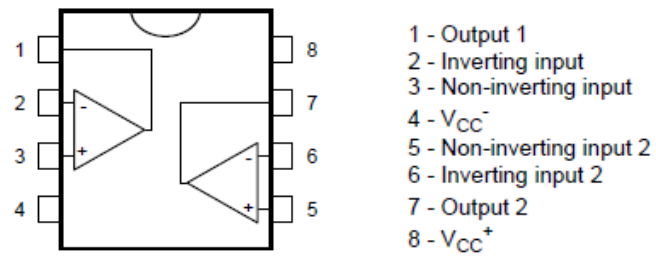


Fig. 3. The pin connections of Op-Amp LM358 (top view)

The data sheet of LM358 is available in the following link:

https://www1.elfa.se/data1/wwwroot/assets/datasheets/jhLM258_e.pdf